

Homework Assignment 1: Answers

Profs. John McLeod & Arash Reyhani

ECE3375, Winter 2022

Problem: Design a memory map for a system with 64 KB of memory. Assume RAM occupies locations between 0x0000 and 0x5FFF (inclusive) and ROM occupies locations between 0xC000 and 0xFFFF (inclusive). Assume you have only the following chips:

- Two (2) 8 K \times 8 ROM chips.
- Two (2) 8 K \times 8 RAM chips.
- Two (2) 4 K \times 8 RAM chips.

In this homework assignment, you must assign an address range to each chip according to the above specifications, and provide the chip select logic.

There is more than one valid solution to this problem.

Solution: The memory range 0x0000 to 0x5FFF spans 24 K, which is the exact amount of RAM available. The four available chips can be inserted into this range in any arbitrary order (this is what is meant by the problems stating that “there is more than one valid solution to this problem”).

- I will put the two big RAM chips at the bottom of this memory range, and the two small RAM chips at the top.


The memory range 0xC000 and 0xFFFF spans 16 K, which is the exact amount of ROM available.

- Here there is no choice on how to arrange the chips, as there is only two identical chips available.

These chips span the following memory range:

Name	Chip	Start Address	End Address
RAM 0	8 K×8	0x0000	0x1FFF
RAM 1	8 K×8	0x2000	0x3FFF
RAM 2	4 K×8	0x4000	0x4FFF
RAM 3	4 K×8	0x5000	0x5FFF
ROM 0	8 K×8	0xC000	0xDFFF
ROM 1	8 K×8	0xE000	0xFFFF

 To design the chip select logic, it should be pretty clear based on the start and end addresses for each chip that only the most significant hex digit will be used for the chip select logic. But I will still write out the full binary address to make sure everything is clear.



Name	Start Address				End Address			
RAM 0	0b0000	0000	0000	0000	0b0001	1111	1111	1111
RAM 1	0b0010	0000	0000	0000	0b0011	1111	1111	1111
RAM 2	0b0100	0000	0000	0000	0b0100	1111	1111	1111
RAM 3	0b0101	0000	0000	0000	0b0101	1111	1111	1111
ROM 0	0b1100	0000	0000	0000	0b1101	1111	1111	1111
ROM 1	0b1110	0000	0000	0000	0b1111	1111	1111	1111

The chip select logic is therefore:

$$CSA_0 = \bar{a}_{15}\bar{a}_{14}\bar{a}_{13}$$

$$CSA_1 = \bar{a}_{15}\bar{a}_{14}a_{13}$$

$$CSA_2 = \bar{a}_{15}a_{14}\bar{a}_{13}\bar{a}_{12}$$

$$CSA_3 = \bar{a}_{15}a_{14}\bar{a}_{13}a_{12}$$

$$CSO_0 = a_{15}a_{14}\bar{a}_{13}$$

$$CSO_0 = a_{15}a_{14}a_{13},$$

where CSA_i stands for “Chip Select RAM i ”, and CSO_i stands for “Chip Select ROM i ”.

Second Solution: It is possible to choose a chip arrangement for RAM that will leave the 8 K \times 8 chips misaligned in memory. This is still a valid memory map, it is just unnecessarily difficult.


- We can put a small RAM chip at the bottom, then a big one, then another small one, then a big one. (There are a few other ways of having misaligned memory chips, this is just one variant.)

It is not possible to misalign the ROM in this problem, so I won't consider that — there is only one valid solution for the ROM as described above. The RAM chips span the following memory range:

Name	Chip	Start Address	End Address
RAM 0	4 K \times 8	0x0000	0x0FFF
RAM 1	8 K \times 8	0x1000	0x2FFF
RAM 2	4 K \times 8	0x3000	0x3FFF
RAM 3	8 K \times 8	0x4000	0x5FFF

The chip select logic is still based on only the most significant hex digit. But again, I will still write out the full binary address to make sure everything is clear.

Name	Start Address				End Address			
RAM 0	0b0000	0000	0000	0000	0b0000	1111	1111	1111
RAM 1	0b0001	0000	0000	0000	0b0010	1111	1111	1111
RAM 2	0b0011	0000	0000	0000	0b0011	1111	1111	1111
RAM 3	0b0100	0000	0000	0000	0b0101	1111	1111	1111

 

The tricky part is RAM 1, which requires 13 bits for addressing the internal memory cells, but the remaining three bits (in red) are not consistent from the start to the end. The solution is straightforward:

- Use the “sum of products” form for the chip select: the logical OR of *two* minterms, each minterm being the entire first 4 bits of the start and end address range.
- This is equivalent to considering the 8 K×8 chip as being two 4 K×8 chips in the same package, so instead of having separate chip selects for each, we have the OR-logic chip select for both together (“RAM 1 = RAM 1a + RAM 1b”).
- Note that this results in bit 12 being used *twice*: as part of the chip select logic, and also passed into the chip’s internal address bus. (Of course this isn’t a problem, just extra wiring.)

Name	Start Address				End Address			
RAM 1a	0b0001	0000	0000	0000	0b0001	1111	1111	1111
RAM 1b	0b0010	0000	0000	0000	0b0010	1111	1111	1111

The chip select logic is therefore:

$$CSA_0 = \bar{a}_{15}\bar{a}_{14}\bar{a}_{13}\bar{a}_{12}$$

$$CSA_1 = \bar{a}_{15}\bar{a}_{14}\bar{a}_{13}a_{12} + \bar{a}_{15}\bar{a}_{14}a_{13}\bar{a}_{12}$$

$$CSA_2 = \bar{a}_{15}\bar{a}_{14}a_{13}a_{12}$$

$$CSA_3 = \bar{a}_{15}a_{14}\bar{a}_{13}.$$

There is almost never a good reason for misaligning a large memory chip like this, so if you are confused by this answer then *just don’t do it*.